

Physics 11

Circuits Unit Retest Solutions

- | | | | | | | | |
|--------|-------------------------------------|----|-------------------------------------|----|-------------------------------------|----|-------------------------------------|
| 1. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 2. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 3. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 4. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 5. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 6. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 7. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 8. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 9. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 10. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 11. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 12. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 13. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 14. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 15. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 16. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 17. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 18. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 19. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 20. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |

1. Problem

The current flowing in an electric circuit can be increased by

- a. increasing voltage and decreasing resistance
- b. decreasing voltage and increasing resistance
- c. increasing voltage and increasing resistance
- d. decreasing voltage and decreasing resistance

Solution

Ohm's law states that

$$I = \frac{V}{R}$$

Therefore, current can be increased by increasing voltage and decreasing resistance.

2. Problem

An ammeter is connected in _____ and a voltmeter is connected in _____.

- a. series, series
- b. series, parallel
- c. parallel, series
- d. parallel, parallel

Solution

An ammeter is connected in series and a voltmeter is connected in parallel.

3. Problem

A battery is rated at 3.7 V and 2100 mAh. How much energy does the battery store at full charge?

- a. 14.7 kJ
- b. 22.4 kJ
- c. 28 kJ
- d. 31.2 kJ

Solution

Convert to SI units and multiply the voltage by the charge:

$$E = QV = (2100 \text{ mAh} \times 3.6 \text{ C/mAh})(3.7 \text{ V}) = 28 \text{ kJ}$$

4. Problem

What voltage is applied across a 2.7Ω resistor if the current is 5.8 A?

- a. 4.8 V
- b. 13 V
- c. 0.44 V
- d. 16 V

Solution

Use Ohm's law:

$$V = IR = (5.8 \text{ A})(2.7 \Omega) = 16 \text{ V}$$

5. Problem

A lamp draws a current of 8.5 A when it is connected to a 6.4 V source. What is the resistance of the lamp?

- a. 1.3Ω
- b. 0.75Ω
- c. 0.67Ω
- d. 54Ω

Solution

Use Ohm's law:

$$R = \frac{V}{I} = \frac{6.4 \text{ V}}{8.5 \text{ A}} = 0.75 \Omega$$

6. Problem

A lamp with a resistance of 6.8Ω is placed across a potential difference of 8.5 V. What is the current through the lamp?

- a. 30 A
- b. 0.8 A
- c. 58 A
- d. 1.2 A

Solution

Use Ohm's law:

$$I = \frac{V}{R} = \frac{8.5 \text{ V}}{6.8 \Omega} = 1.2 \text{ A}$$

7. Problem

A voltage source of 6.1 V delivers a current of 6.2 A to an electric motor that is connected across its terminals. What power is consumed by the motor?

- a. 66 W
- b. 0.98 W
- c. 62 W
- d. 38 W

Solution

Use the formula for the power in a circuit:

$$P = IV = (6.2 \text{ A})(6.1 \text{ V}) = 38 \text{ W}$$

8. Problem

An electronic device is powered by a 4.4 V battery. The current used to operate the device is 190 mA. How much energy does the device use in 9.4 minutes?

- a. 7.9 J
- b. 470 J
- c. 110 J
- d. 7900 J

Solution

Find the power of the device using $P = IV$ and multiply by the time. Remember to convert all units.

$$E = Pt = IVt = (0.19 \text{ A})(4.4 \text{ V})(9.4 \times 60 \text{ s}) = 470 \text{ J}$$

9. Problem

As more resistors are added in **series** to a constant voltage source, the power supplied by the source

- a. increases.
- b. decreases.
- c. remains the same.
- d. not enough information.

Solution

The total resistance increases, causing the total current to decrease. Since the voltage is constant and $P = IV$, the power decreases.

10. Problem

Three resistors are connected in **series**. Their resistances are 33Ω , 66Ω , and 78Ω . What is the equivalent resistance of the resistors?

- a. 95Ω
- b. 160Ω
- c. 220Ω
- d. 180Ω

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 177 \Omega$$

11. Problem

When different resistors are connected in parallel, it is true that

- a. the power dissipated in each is the same.
- b. the potential difference across each is the same.
- c. their equivalent resistance is greater than the resistance of one of the resistors.
- d. the same current flows in each one.

Solution

The potential difference is the same across resistors in parallel.

12. Problem

You have a 60 W light bulb and a 100 W light bulb. Instead of connecting them the normal way, you make a circuit that places them in series across the normal household voltage. Which statement is correct?

- a. Both bulbs glow at the same reduced brightness.
- b. Both bulbs glow at the same increased brightness.
- c. The 100 W bulb glows brighter than the 60 W bulb.
- d. The 60 W bulb glows brighter than the 100 W bulb.

Solution

The 60 W bulb has a higher resistance than the 100 W, which is why it is normally dimmer (bulbs are normally connected in parallel). However, when the two bulbs are connected in series, there is a greater voltage drop across the 60 W, making it brighter (the current is the same for bulbs in series).

13. Problem

A total of 495 resistors, all with resistance $147\ \Omega$, are connected in **parallel**. What is the equivalent resistance of the resistors?

- a. $0.3\ \Omega$
- b. $0.38\ \Omega$
- c. $0.41\ \Omega$
- d. $0.34\ \Omega$

Solution

The equivalent resistance of resistors in parallel when they all have the same resistance R_i is

$$R = \left(\frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_i} + \dots \right)^{-1} = \frac{R_i}{495} = 0.3\ \Omega$$

14. Problem

A total of 169 Christmas light bulbs, all with resistance $0.52\ \Omega$, are connected in **series**. What is the equivalent resistance of the lights?

- a. $88\ \Omega$
- b. $110\ \Omega$
- c. $120\ \Omega$
- d. $50\ \Omega$

Solution

The equivalent resistance of resistors in series when they all have the same resistance R_i is

$$R = R_i + R_i + R_i + \dots + R_i = 169R_i = 88\ \text{k}\Omega$$

15. Problem

Two resistors are connected in **parallel**. Their resistances are $220\ \Omega$ and $415\ \Omega$. A battery applies $4.2\ \text{V}$ to the combination. What is the current through the $220\ \Omega$ resistor?

- a. $16\ \text{mA}$
- b. $19\ \text{mA}$
- c. $14\ \text{mA}$
- d. $12\ \text{mA}$

Solution

The full voltage of the battery is applied to both resistors. The current through the first resistor is

$$I = \frac{V}{R} = \frac{4.2\ \text{V}}{220\ \Omega} = 19\ \text{mA}$$

16. Problem

Two resistors are connected in **series**. Their resistances are $4\ \Omega$ and $1\ \Omega$. A difference in potential of $18\ \text{V}$ is applied to the combination. What is the current through the $1\ \Omega$ resistor?

- a. $2.8\ \text{A}$
- b. $2.4\ \text{A}$
- c. $3.6\ \text{A}$
- d. $3.2\ \text{A}$

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 5\ \Omega$$

The current is the same through all components in series and its value is

$$I = \frac{V}{R} = \frac{18\ \text{V}}{5\ \Omega} = 3.6\ \text{A}$$

17. Problem

Two resistors are connected in **parallel**. Their resistances are $36\ \Omega$ and $37\ \Omega$. A battery applies $16\ \text{V}$ to the combination. What is the current drawn from the battery?

- a. $1.6\ \text{A}$
- b. $1.2\ \text{A}$
- c. $0.88\ \text{A}$
- d. $1\ \text{A}$

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 18.2465753\ \Omega$$

The current drawn from the battery is

$$I = \frac{V}{R} = \frac{16 \text{ V}}{18.2465753 \Omega} = 0.88 \text{ A}$$

18. Problem

Three resistors are connected in **parallel**. Their resistances are 52Ω , 61Ω , and 79Ω . What is the equivalent resistance of the resistors?

- a. 14Ω
- b. 19Ω
- c. 21Ω
- d. 16Ω

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 21 \Omega$$

19. Problem

A 400 mA current flows into a parallel combination of a 93Ω and a 71Ω resistor. What current flows through the 93Ω resistor?

- a. 150 mA
- b. 170 mA
- c. 140 mA
- d. 310 mA

Solution

The total current is equal to the sum of the current through each resistor

$$I = I_1 + I_2$$

The voltage across each resistor is the same and $V = IR$ so

$$I_1 R_1 = I_2 R_2$$

Combining the two equations and solving for I_1 gives

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I = 170 \text{ mA}$$

20. Problem

When a battery with an emf of 2.5 V supplies a 0.39 A current, its terminal voltage is 1.2 V. What is the internal resistance of the battery?

- a. $2.5\ \Omega$
- b. $6.5\ \Omega$
- c. $4.2\ \Omega$
- d. $3.3\ \Omega$

Solution

The terminal resistance is related to the emf by $V_{\text{terminal}} = \mathcal{E} - Ir$. Therefore,

$$r = \frac{\mathcal{E} - V_{\text{terminal}}}{I} = 3.3\ \Omega$$