

Physics 11

Circuits Unit Test Solutions

1. a. ☐ b. ☐ c. ☒ d. ☐
2. a. ☒ b. ☐ c. ☐ d. ☐
3. a. ☐ b. ☒ c. ☐ d. ☐
4. a. ☐ b. ☒ c. ☐ d. ☐
5. a. ☒ b. ☐ c. ☐ d. ☐
6. a. ☐ b. ☐ c. ☐ d. ☒
7. a. ☒ b. ☐ c. ☐ d. ☐
8. a. ☐ b. ☒ c. ☐ d. ☐
9. a. ☐ b. ☒ c. ☐ d. ☐
10. a. ☐ b. ☐ c. ☐ d. ☒
11. a. ☐ b. ☐ c. ☒ d. ☐
12. a. ☐ b. ☒ c. ☐ d. ☐
13. a. ☐ b. ☐ c. ☒ d. ☐
14. a. ☐ b. ☐ c. ☒ d. ☐
15. a. ☐ b. ☐ c. ☒ d. ☐
16. a. ☐ b. ☒ c. ☐ d. ☐
17. a. ☐ b. ☒ c. ☐ d. ☐
18. a. ☐ b. ☒ c. ☐ d. ☐
19. a. ☒ b. ☐ c. ☐ d. ☐
20. a. ☐ b. ☒ c. ☐ d. ☐

1. Problem

Which device can be used to measure the current in a circuit?

- a. voltmeter
- b. ohmmeter
- c. ammeter
- d. currentometer

Solution

Current can be measured by an ammeter.

2. Problem

Car batteries are rated in “amp-hours”. This is a measure of their

- a. electric charge
- b. current
- c. energy density
- d. energy capacity

Solution

The amp-hour comes from multiplying current and time and is therefore a unit of electric charge.

3. Problem

A battery is rated at 12 V and 1100 mAh. How much energy does the battery store at full charge?

- a. 88.4 kJ
- b. 48 kJ
- c. 41 kJ
- d. 27.9 kJ

Solution

Convert to SI units and multiply the voltage by the charge:

$$E = QV = (1100 \text{ mAh} \times 3.6 \text{ C/mAh})(12 \text{ V}) = 48 \text{ kJ}$$

4. Problem

What voltage is applied across a 4Ω resistor if the current is 7.8 A?

- a. 40 V
- b. 31 V
- c. 2 V
- d. 6.6 V

Solution

Use Ohm's law:

$$V = IR = (7.8 \text{ A})(4 \Omega) = 31 \text{ V}$$

5. Problem

A lamp draws a current of 8 A when it is connected to a 7.5 V source. What is the resistance of the lamp?

- a. $0.94\ \Omega$
- b. $16\ \Omega$
- c. $1.1\ \Omega$
- d. $60\ \Omega$

Solution

Use Ohm's law:

$$R = \frac{V}{I} = \frac{7.5\text{ V}}{8\text{ A}} = 0.94\ \Omega$$

6. Problem

A lamp with a resistance of $6.8\ \Omega$ is placed across a potential difference of 8.5 V. What is the current through the lamp?

- a. 0.65 A
- b. 0.8 A
- c. 0.96 A
- d. 1.2 A

Solution

Use Ohm's law:

$$I = \frac{V}{R} = \frac{8.5\text{ V}}{6.8\ \Omega} = 1.2\text{ A}$$

7. Problem

A voltage source of 8 V delivers a current of 5.3 A to an electric motor that is connected across its terminals. What power is consumed by the motor?

- a. 42 W
- b. 37 W
- c. 29 W
- d. 7 W

Solution

Use the formula for the power in a circuit:

$$P = IV = (5.3\text{ A})(8\text{ V}) = 42\text{ W}$$

8. Problem

A space heater with a resistance of $9.3\ \Omega$ operates at a voltage of 117 V . How much energy does the space heater use in 9.1 hours?

- a. 6.7 kWh
- b. 13 kWh
- c. 8.2 kWh
- d. 9.6 kWh

Solution

Find the power of the device using $P = IV = V^2/R$ and multiply by the time. Remember to convert all units.

$$E = Pt = \frac{V^2}{R}t = \frac{(117\text{ V})^2}{9.3\ \Omega}(9.1\text{ h}) = 13000\text{ Wh} = 13\text{ kWh}$$

9. Problem

As more resistors are added in **series** to a constant voltage source, the power supplied by the source

- a. increases.
- b. decreases.
- c. remains the same.
- d. not enough information.

Solution

The total resistance increases, causing the total current to decrease. Since the voltage is constant and $P = IV$, the power decreases.

10. Problem

Three resistors are connected in **series**. Their resistances are $68\ \Omega$, $60\ \Omega$, and $38\ \Omega$. What is the equivalent resistance of the resistors?

- a. $17\ \Omega$
- b. $140\ \Omega$
- c. $320\ \Omega$
- d. $170\ \Omega$

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 166\ \Omega$$

11. Problem

When different resistors are connected in series, it is true that

- a. the potential difference across each is the same.
- b. the power dissipated in each is the same.
- c. the same current flows in each one.
- d. the total resistance is equal to the greatest resistance of any individual resistor.

Solution

The current is the same in resistors in series.

12. Problem

You have a $5\ \Omega$ light bulb and a $10\ \Omega$ light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?

- a. The $5\ \Omega$ bulb is brighter.
- b. The $10\ \Omega$ bulb is brighter.
- c. Both bulbs glow at the same brightness.
- d. It depends on the voltage.

Solution

The current through both bulbs is the same since they are placed in series. However, the voltage drop is greater for the greater resistance. Since $P = IV$, and V is greater for the greater resistance, the $10\ \Omega$ light bulb is brighter.

13. Problem

A total of 993 resistors, all with resistance $765\ \Omega$, are connected in **parallel**. What is the equivalent resistance of the resistors?

- a. $0.5\ \Omega$
- b. $0.59\ \Omega$
- c. $0.77\ \Omega$
- d. $0.41\ \Omega$

Solution

The equivalent resistance of resistors in parallel when they all have the same resistance R_i is

$$R = \left(\frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_i} + \dots \right)^{-1} = \frac{R_i}{993} = 0.77\ \Omega$$

14. Problem

A total of 945 Christmas light bulbs, all with resistance $817\ \Omega$, are connected in **series**. What is the equivalent resistance of the lights?

- a. $850\ \text{k}\Omega$
- b. $1100\ \text{k}\Omega$
- c. $770\ \text{k}\Omega$
- d. $960\ \text{k}\Omega$

Solution

The equivalent resistance of resistors in series when they all have the same resistance R_i is

$$R = R_i + R_i + R_i + \dots + R_i = 945R_i = 770\ \text{k}\Omega$$

15. Problem

Two resistors are connected in **parallel**. Their resistances are $465\ \Omega$ and $414\ \Omega$. A battery applies $1.6\ \text{V}$ to the combination. What is the current through the $465\ \Omega$ resistor?

- a. $3.8\ \text{mA}$
- b. $2.2\ \text{mA}$
- c. $3.4\ \text{mA}$
- d. $5.5\ \text{mA}$

Solution

The full voltage of the battery is applied to both resistors. The current through the first resistor is

$$I = \frac{V}{R} = \frac{1.6\ \text{V}}{465\ \Omega} = 3.4\ \text{mA}$$

16. Problem

Two resistors are connected in **series**. Their resistances are $5\ \Omega$ and $8\ \Omega$. A difference in potential of $31\ \text{V}$ is applied to the combination. What is the current through the $8\ \Omega$ resistor?

- a. $1.5\ \text{A}$
- b. $2.4\ \text{A}$
- c. $2.1\ \text{A}$
- d. $3.2\ \text{A}$

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 13\ \Omega$$

The current is the same through all components in series and its value is

$$I = \frac{V}{R} = \frac{31\ \text{V}}{13\ \Omega} = 2.4\ \text{A}$$

17. Problem

Two resistors are connected in **parallel**. Their resistances are $15\ \Omega$ and $35\ \Omega$. A battery applies $95\ \text{V}$ to the combination. What is the current drawn from the battery?

- a. $7.7\ \text{A}$
- b. $9\ \text{A}$
- c. $14\ \text{A}$
- d. $11\ \text{A}$

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 10.5\ \Omega$$

The current drawn from the battery is

$$I = \frac{V}{R} = \frac{95 \text{ V}}{10.5 \Omega} = 9 \text{ A}$$

18. Problem

Three resistors are connected in **parallel**. Their resistances are 28Ω , 89Ω , and 33Ω . What is the equivalent resistance of the resistors?

- a. 17Ω
- b. 13Ω
- c. 22Ω
- d. 9.3Ω

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 13 \Omega$$

19. Problem

A 600 mA current flows into a parallel combination of a 95Ω and a 67Ω resistor. What current flows through the 95Ω resistor?

- a. 250 mA
- b. 170 mA
- c. 370 mA
- d. 340 mA

Solution

The total current is equal to the sum of the current through each resistor

$$I = I_1 + I_2$$

The voltage across each resistor is the same and $V = IR$ so

$$I_1 R_1 = I_2 R_2$$

Combining the two equations and solving for I_1 gives

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I = 250 \text{ mA}$$

20. Problem

When a battery with an emf of 9.7 V supplies a 1.7 A current, its terminal voltage is 5.9 V. What is the internal resistance of the battery?

- a. $4.2\ \Omega$
- b. $2.2\ \Omega$
- c. $3.9\ \Omega$
- d. $1.5\ \Omega$

Solution

The terminal resistance is related to the emf by $V_{\text{terminal}} = \mathcal{E} - Ir$. Therefore,

$$r = \frac{\mathcal{E} - V_{\text{terminal}}}{I} = 2.2\ \Omega$$