



# McRoberts Secondary

Circuits Unit Test 2025-12-17



## Personal Data

Family Name:
Given Name:
Signature:
checked

## Registration Number

--	--	--	--	--	--	--	--

0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	0
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	1
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	2
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	3
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	4
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	5
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	6
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	7
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	8
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	9

In this section **no** changes or modifications must be made!

Scrambling

0 0

Type

020

Exam ID(Physics 11)

25121700004

Please mark the boxes carefully: ☒ Not marked: ☐ or ☐

This document is scanned automatically. Please keep clean and do not bend or fold. For filling in the document please use a **blue or black pen**.

**Only clearly marked and positionally accurate crosses will be processed!**

## Answers 1 - 15

	a	b	c	d
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
11	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
12	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
13	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
14	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
15	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

a b c d

## Answers 16 - 20

	a	b	c	d
16	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
17	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
18	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
19	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
20	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

a b c d





1. Which device can be used to measure the current in a circuit?
  - a. ohmmeter
  - b. currentometer
  - c. ammeter
  - d. potentiometer
2. Car batteries are rated in "amp-hours". This is a measure of their
  - a. electric charge
  - b. current
  - c. energy capacity
  - d. power
3. A battery is rated at 6.8 V and 2900 mAh. How much energy does the battery store at full charge?
  - a. 106 kJ
  - b. 114 kJ
  - c. 71 kJ
  - d. 83.4 kJ
4. What voltage is applied across a  $7\ \Omega$  resistor if the current is 8.3 A?
  - a. 97 V
  - b. 11 V
  - c. 50 V
  - d. 58 V
5. A lamp draws a current of 4.3 A when it is connected to a 5.9 V source. What is the resistance of the lamp?
  - a.  $21\ \Omega$
  - b.  $0.73\ \Omega$
  - c.  $25\ \Omega$
  - d.  $1.4\ \Omega$
6. A lamp with a resistance of  $6.8\ \Omega$  is placed across a potential difference of 8.5 V. What is the current through the lamp?
  - a. 1.2 A
  - b. 14 A
  - c. 58 A
  - d. 28 A
7. A voltage source of 8.7 V delivers a current of 1.8 A to an electric motor that is connected across its terminals. What power is consumed by the motor?
  - a. 16 W
  - b. 9.6 W
  - c. 4.8 W
  - d. 13 W

8. An electronic device is powered by a 4.1 V battery. The current used to operate the device is 210 mA. How much energy does the device use in 8.9 minutes?
- 380 J
  - 460 J
  - 7.7 J
  - 7700 J
9. As more resistors are added in **series** to a constant voltage source, the power supplied by the source
- increases.
  - decreases.
  - remains the same.
  - not enough information.
10. Three resistors are connected in **series**. Their resistances are  $74\ \Omega$ ,  $30\ \Omega$ , and  $10\ \Omega$ . What is the equivalent resistance of the resistors?
- $190\ \Omega$
  - $210\ \Omega$
  - $110\ \Omega$
  - $6.8\ \Omega$
11. When different resistors are connected in parallel, it is true that
- the potential difference across each is the same.
  - their equivalent resistance is greater than the resistance of one of the resistors.
  - the power dissipated in each is the same.
  - the same current flows in each one.
12. You have a  $5\ \Omega$  light bulb and a  $10\ \Omega$  light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?
- The  $5\ \Omega$  bulb is brighter.
  - The  $10\ \Omega$  bulb is brighter.
  - Both bulbs glow at the same brightness.
  - It depends on the voltage.
13. A total of 757 resistors, all with resistance  $796\ \Omega$ , are connected in **parallel**. What is the equivalent resistance of the resistors?
- $1.6\ \Omega$
  - $1.4\ \Omega$
  - $1.2\ \Omega$
  - $1.1\ \Omega$
14. A total of 279 Christmas light bulbs, all with resistance  $672\ \Omega$ , are connected in **series**. What is the equivalent resistance of the lights?
- $210\ \text{k}\Omega$
  - $170\ \text{k}\Omega$
  - $190\ \text{k}\Omega$
  - $280\ \text{k}\Omega$

15. Two resistors are connected in **parallel**. Their resistances are  $468\ \Omega$  and  $432\ \Omega$ . A battery applies  $4.5\ \text{V}$  to the combination. What is the current through the  $468\ \Omega$  resistor?
- $9.6\ \text{mA}$
  - $5.1\ \text{mA}$
  - $7.3\ \text{mA}$
  - $8.5\ \text{mA}$
16. Two resistors are connected in **series**. Their resistances are  $8\ \Omega$  and  $4\ \Omega$ . A difference in potential of  $85\ \text{V}$  is applied to the combination. What is the current through the  $4\ \Omega$  resistor?
- $9.3\ \text{A}$
  - $11\ \text{A}$
  - $4.3\ \text{A}$
  - $7.1\ \text{A}$
17. Two resistors are connected in **parallel**. Their resistances are  $40\ \Omega$  and  $39\ \Omega$ . A battery applies  $95\ \text{V}$  to the combination. What is the current drawn from the battery?
- $3.2\ \text{A}$
  - $3.7\ \text{A}$
  - $4.8\ \text{A}$
  - $2.7\ \text{A}$
18. Three resistors are connected in **parallel**. Their resistances are  $33\ \Omega$ ,  $100\ \Omega$ , and  $57\ \Omega$ . What is the equivalent resistance of the resistors?
- $25\ \Omega$
  - $8.7\ \Omega$
  - $17\ \Omega$
  - $13\ \Omega$
19. A  $700\ \text{mA}$  current flows into a parallel combination of a  $27\ \Omega$  and a  $10\ \Omega$  resistor. What current flows through the  $27\ \Omega$  resistor?
- $240\ \text{mA}$
  - $190\ \text{mA}$
  - $130\ \text{mA}$
  - $95\ \text{mA}$
20. When a battery with an emf of  $6\ \text{V}$  supplies a  $8\ \text{A}$  current, its terminal voltage is  $4.8\ \text{V}$ . What is the internal resistance of the battery?
- $0.17\ \Omega$
  - $0.087\ \Omega$
  - $0.21\ \Omega$
  - $0.15\ \Omega$