

Physics 11

Circuits Unit Retest Solutions

1. a. ☒ b. ☐ c. ☐ d. ☐
2. a. ☐ b. ☒ c. ☐ d. ☐
3. a. ☐ b. ☐ c. ☐ d. ☒
4. a. ☒ b. ☐ c. ☐ d. ☐
5. a. ☒ b. ☐ c. ☐ d. ☐
6. a. ☐ b. ☐ c. ☐ d. ☒
7. a. ☐ b. ☐ c. ☐ d. ☒
8. a. ☐ b. ☐ c. ☒ d. ☐
9. a. ☐ b. ☒ c. ☐ d. ☐
10. a. ☒ b. ☐ c. ☐ d. ☐
11. a. ☐ b. ☐ c. ☐ d. ☒
12. a. ☐ b. ☐ c. ☐ d. ☒
13. a. ☐ b. ☒ c. ☐ d. ☐
14. a. ☐ b. ☐ c. ☐ d. ☒
15. a. ☒ b. ☐ c. ☐ d. ☐
16. a. ☒ b. ☐ c. ☐ d. ☐
17. a. ☐ b. ☒ c. ☐ d. ☐
18. a. ☐ b. ☒ c. ☐ d. ☐
19. a. ☐ b. ☐ c. ☒ d. ☐
20. a. ☐ b. ☒ c. ☐ d. ☐

1. Problem

The current flowing in an electric circuit can be increased by

- a. increasing voltage and decreasing resistance
- b. decreasing voltage and increasing resistance
- c. increasing voltage and increasing resistance
- d. decreasing voltage and decreasing resistance

Solution

Ohm's law states that

$$I = \frac{V}{R}$$

Therefore, current can be increased by increasing voltage and decreasing resistance.

2. Problem

An ammeter is connected in _____ and a voltmeter is connected in _____.

- a. series, series
- b. series, parallel
- c. parallel, series
- d. parallel, parallel

Solution

An ammeter is connected in series and a voltmeter is connected in parallel.

3. Problem

A battery is rated at 10 V and 5600 mAh. How much energy does the battery store at full charge?

- a. 105 kJ
- b. 174 kJ
- c. 346 kJ
- d. 200 kJ

Solution

Convert to SI units and multiply the voltage by the charge:

$$E = QV = (5600 \text{ mAh} \times 3.6 \text{ C/mAh})(10 \text{ V}) = 200 \text{ kJ}$$

4. Problem

What voltage is applied across a 3.6Ω resistor if the current is 5.9 A?

- a. 21 V
- b. 19 V
- c. 1.6 V
- d. 12 V

Solution

Use Ohm's law:

$$V = IR = (5.9 \text{ A})(3.6 \Omega) = 21 \text{ V}$$

5. Problem

A lamp draws a current of 9.7 A when it is connected to a 4.9 V source. What is the resistance of the lamp?

- a. 0.51Ω
- b. 2Ω
- c. 0.39Ω
- d. 0.27Ω

Solution

Use Ohm's law:

$$R = \frac{V}{I} = \frac{4.9 \text{ V}}{9.7 \text{ A}} = 0.51 \Omega$$

6. Problem

A lamp with a resistance of 6.8Ω is placed across a potential difference of 8.5 V. What is the current through the lamp?

- a. 17 A
- b. 58 A
- c. 0.68 A
- d. 1.2 A

Solution

Use Ohm's law:

$$I = \frac{V}{R} = \frac{8.5 \text{ V}}{6.8 \Omega} = 1.2 \text{ A}$$

7. Problem

A voltage source of 6.4 V delivers a current of 2.1 A to an electric motor that is connected across its terminals. What power is consumed by the motor?

- a. 3 W
- b. 11 W
- c. 16 W
- d. 13 W

Solution

Use the formula for the power in a circuit:

$$P = IV = (2.1 \text{ A})(6.4 \text{ V}) = 13 \text{ W}$$

8. Problem

An electronic device is powered by a 3.5 V battery. The current used to operate the device is 200 mA. How much energy does the device use in 6 minutes?

- a. 4200 J
- b. 4.2 J
- c. 250 J
- d. 140 J

Solution

Find the power of the device using $P = IV$ and multiply by the time. Remember to convert all units.

$$E = Pt = IVt = (0.2 \text{ A})(3.5 \text{ V})(6 \times 60 \text{ s}) = 250 \text{ J}$$

9. Problem

As more resistors are added in **series** to a constant voltage source, the power supplied by the source

- a. increases.
- b. decreases.
- c. remains the same.
- d. not enough information.

Solution

The total resistance increases, causing the total current to decrease. Since the voltage is constant and $P = IV$, the power decreases.

10. Problem

Three resistors are connected in **series**. Their resistances are 82Ω , 42Ω , and 28Ω . What is the equivalent resistance of the resistors?

- a. 150Ω
- b. 53Ω
- c. 170Ω
- d. 270Ω

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 152 \Omega$$

11. Problem

When different resistors are connected in parallel, it is true that

- a. the same current flows in each one.
- b. their equivalent resistance is greater than the resistance of one of the resistors.
- c. the power dissipated in each is the same.
- d. the potential difference across each is the same.

Solution

The potential difference is the same across resistors in parallel.

12. Problem

You have a 60 W light bulb and a 100 W light bulb. Instead of connecting them the normal way, you make a circuit that places them in series across the normal household voltage. Which statement is correct?

- a. Both bulbs glow at the same reduced brightness.
- b. Both bulbs glow at the same increased brightness.
- c. The 100 W bulb glows brighter than the 60 W bulb.
- d. The 60 W bulb glows brighter than the 100 W bulb.

Solution

The 60 W bulb has a higher resistance than the 100 W, which is why it is normally dimmer (bulbs are normally connected in parallel). However, when the two bulbs are connected in series, there is a greater voltage drop across the 60 W, making it brighter (the current is the same for bulbs in series).

13. Problem

A total of 799 resistors, all with resistance $569\ \Omega$, are connected in **parallel**. What is the equivalent resistance of the resistors?

- a. $0.46\ \Omega$
- b. $0.71\ \Omega$
- c. $0.62\ \Omega$
- d. $0.36\ \Omega$

Solution

The equivalent resistance of resistors in parallel when they all have the same resistance R_i is

$$R = \left(\frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_i} + \dots \right)^{-1} = \frac{R_i}{799} = 0.71\ \Omega$$

14. Problem

A total of 703 Christmas light bulbs, all with resistance $0.628\ \Omega$, are connected in **series**. What is the equivalent resistance of the lights?

- a. $620\ \Omega$
- b. $490\ \Omega$
- c. $540\ \Omega$
- d. $440\ \Omega$

Solution

The equivalent resistance of resistors in series when they all have the same resistance R_i is

$$R = R_i + R_i + R_i + \dots + R_i = 703R_i = 440\ \text{k}\Omega$$

15. Problem

Two resistors are connected in **parallel**. Their resistances are $347\ \Omega$ and $323\ \Omega$. A battery applies 1.7 V to the combination. What is the current through the $347\ \Omega$ resistor?

- a. 4.9 mA
- b. 4.2 mA
- c. 8.4 mA
- d. 3.5 mA

Solution

The full voltage of the battery is applied to both resistors. The current through the first resistor is

$$I = \frac{V}{R} = \frac{1.7\text{ V}}{347\ \Omega} = 4.9\text{ mA}$$

16. Problem

Two resistors are connected in **series**. Their resistances are $4\ \Omega$ and $3\ \Omega$. A difference in potential of 68 V is applied to the combination. What is the current through the $3\ \Omega$ resistor?

- a. 9.7 A
- b. 5.3 A
- c. 7 A
- d. 8.5 A

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 7\ \Omega$$

The current is the same through all components in series and its value is

$$I = \frac{V}{R} = \frac{68\text{ V}}{7\ \Omega} = 9.7\text{ A}$$

17. Problem

Two resistors are connected in **parallel**. Their resistances are $16\ \Omega$ and $18\ \Omega$. A battery applies 56 V to the combination. What is the current drawn from the battery?

- a. 11 A
- b. 6.6 A
- c. 9.1 A
- d. 3.7 A

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 8.4705882\ \Omega$$

The current drawn from the battery is

$$I = \frac{V}{R} = \frac{56 \text{ V}}{8.4705882 \Omega} = 6.6 \text{ A}$$

18. Problem

Three resistors are connected in **parallel**. Their resistances are 78Ω , 45Ω , and 70Ω . What is the equivalent resistance of the resistors?

- a. 15Ω
- b. 20Ω
- c. 18Ω
- d. 40Ω

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 20 \Omega$$

19. Problem

A 800 mA current flows into a parallel combination of a 82Ω and a 48Ω resistor. What current flows through the 82Ω resistor?

- a. 170 mA
- b. 460 mA
- c. 300 mA
- d. 240 mA

Solution

The total current is equal to the sum of the current through each resistor

$$I = I_1 + I_2$$

The voltage across each resistor is the same and $V = IR$ so

$$I_1 R_1 = I_2 R_2$$

Combining the two equations and solving for I_1 gives

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I = 300 \text{ mA}$$

20. Problem

When a battery with an emf of 7 V supplies a 0.31 A current, its terminal voltage is 5.9 V. What is the internal resistance of the battery?

- a. $3.1\ \Omega$
- b. $3.5\ \Omega$
- c. $2.4\ \Omega$
- d. $5.3\ \Omega$

Solution

The terminal resistance is related to the emf by $V_{\text{terminal}} = \mathcal{E} - Ir$. Therefore,

$$r = \frac{\mathcal{E} - V_{\text{terminal}}}{I} = 3.5\ \Omega$$