

Physics 11

Circuits Unit Test Solutions

1. a. ☐ b. ☐ c. ☒ d. ☐
2. a. ☒ b. ☐ c. ☐ d. ☐
3. a. ☐ b. ☐ c. ☒ d. ☐
4. a. ☐ b. ☐ c. ☐ d. ☒
5. a. ☐ b. ☐ c. ☐ d. ☒
6. a. ☒ b. ☐ c. ☐ d. ☐
7. a. ☒ b. ☐ c. ☐ d. ☐
8. a. ☐ b. ☒ c. ☐ d. ☐
9. a. ☐ b. ☒ c. ☐ d. ☐
10. a. ☐ b. ☐ c. ☒ d. ☐
11. a. ☒ b. ☐ c. ☐ d. ☐
12. a. ☐ b. ☒ c. ☐ d. ☐
13. a. ☐ b. ☐ c. ☐ d. ☒
14. a. ☐ b. ☐ c. ☒ d. ☐
15. a. ☒ b. ☐ c. ☐ d. ☐
16. a. ☐ b. ☐ c. ☐ d. ☒
17. a. ☐ b. ☐ c. ☒ d. ☐
18. a. ☐ b. ☐ c. ☒ d. ☐
19. a. ☐ b. ☒ c. ☐ d. ☐
20. a. ☐ b. ☐ c. ☐ d. ☒

1. Problem

Which device can be used to measure the current in a circuit?

- a. ohmmeter
- b. currentometer
- c. ammeter
- d. potentiometer

Solution

Current can be measured by an ammeter.

2. Problem

Car batteries are rated in “amp-hours”. This is a measure of their

- a. electric charge
- b. current
- c. energy capacity
- d. power

Solution

The amp-hour comes from multiplying current and time and is therefore a unit of electric charge.

3. Problem

A battery is rated at 6.8 V and 2900 mAh. How much energy does the battery store at full charge?

- a. 106 kJ
- b. 114 kJ
- c. 71 kJ
- d. 83.4 kJ

Solution

Convert to SI units and multiply the voltage by the charge:

$$E = QV = (2900 \text{ mAh} \times 3.6 \text{ C/mAh})(6.8 \text{ V}) = 71 \text{ kJ}$$

4. Problem

What voltage is applied across a 7Ω resistor if the current is 8.3 A?

- a. 97 V
- b. 11 V
- c. 50 V
- d. 58 V

Solution

Use Ohm's law:

$$V = IR = (8.3 \text{ A})(7 \Omega) = 58 \text{ V}$$

5. Problem

A lamp draws a current of 4.3 A when it is connected to a 5.9 V source. What is the resistance of the lamp?

- a. $21\ \Omega$
- b. $0.73\ \Omega$
- c. $25\ \Omega$
- d. $1.4\ \Omega$

Solution

Use Ohm's law:

$$R = \frac{V}{I} = \frac{5.9\text{ V}}{4.3\text{ A}} = 1.4\ \Omega$$

6. Problem

A lamp with a resistance of $6.8\ \Omega$ is placed across a potential difference of 8.5 V. What is the current through the lamp?

- a. 1.2 A
- b. 14 A
- c. 58 A
- d. 28 A

Solution

Use Ohm's law:

$$I = \frac{V}{R} = \frac{8.5\text{ V}}{6.8\ \Omega} = 1.2\text{ A}$$

7. Problem

A voltage source of 8.7 V delivers a current of 1.8 A to an electric motor that is connected across its terminals. What power is consumed by the motor?

- a. 16 W
- b. 9.6 W
- c. 4.8 W
- d. 13 W

Solution

Use the formula for the power in a circuit:

$$P = IV = (1.8\text{ A})(8.7\text{ V}) = 16\text{ W}$$

8. Problem

An electronic device is powered by a 4.1 V battery. The current used to operate the device is 210 mA. How much energy does the device use in 8.9 minutes?

- a. 380 J
- b. 460 J
- c. 7.7 J
- d. 7700 J

Solution

Find the power of the device using $P = IV$ and multiply by the time. Remember to convert all units.

$$E = Pt = IVt = (0.21 \text{ A})(4.1 \text{ V})(8.9 \times 60 \text{ s}) = 460 \text{ J}$$

9. Problem

As more resistors are added in **series** to a constant voltage source, the power supplied by the source

- a. increases.
- b. decreases.
- c. remains the same.
- d. not enough information.

Solution

The total resistance increases, causing the total current to decrease. Since the voltage is constant and $P = IV$, the power decreases.

10. Problem

Three resistors are connected in **series**. Their resistances are 74Ω , 30Ω , and 10Ω . What is the equivalent resistance of the resistors?

- a. 190Ω
- b. 210Ω
- c. 110Ω
- d. 6.8Ω

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 114 \Omega$$

11. Problem

When different resistors are connected in parallel, it is true that

- a. the potential difference across each is the same.
- b. their equivalent resistance is greater than the resistance of one of the resistors.
- c. the power dissipated in each is the same.
- d. the same current flows in each one.

Solution

The potential difference is the same across resistors in parallel.

12. Problem

You have a $5\ \Omega$ light bulb and a $10\ \Omega$ light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?

- a. The $5\ \Omega$ bulb is brighter.
- b. The $10\ \Omega$ bulb is brighter.
- c. Both bulbs glow at the same brightness.
- d. It depends on the voltage.

Solution

The current through both bulbs is the same since they are placed in series. However, the voltage drop is greater for the greater resistance. Since $P = IV$, and V is greater for the greater resistance, the $10\ \Omega$ light bulb is brighter.

13. Problem

A total of 757 resistors, all with resistance $796\ \Omega$, are connected in **parallel**. What is the equivalent resistance of the resistors?

- a. $1.6\ \Omega$
- b. $1.4\ \Omega$
- c. $1.2\ \Omega$
- d. $1.1\ \Omega$

Solution

The equivalent resistance of resistors in parallel when they all have the same resistance R_i is

$$R = \left(\frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_i} + \dots \right)^{-1} = \frac{R_i}{757} = 1.1\ \Omega$$

14. Problem

A total of 279 Christmas light bulbs, all with resistance $672\ \Omega$, are connected in **series**. What is the equivalent resistance of the lights?

- a. $210\ \text{k}\Omega$
- b. $170\ \text{k}\Omega$
- c. $190\ \text{k}\Omega$
- d. $280\ \text{k}\Omega$

Solution

The equivalent resistance of resistors in series when they all have the same resistance R_i is

$$R = R_i + R_i + R_i + \dots + R_i = 279R_i = 190\ \text{k}\Omega$$

15. Problem

Two resistors are connected in **parallel**. Their resistances are $468\ \Omega$ and $432\ \Omega$. A battery applies 4.5 V to the combination. What is the current through the $468\ \Omega$ resistor?

- a. 9.6 mA
- b. 5.1 mA
- c. 7.3 mA
- d. 8.5 mA

Solution

The full voltage of the battery is applied to both resistors. The current through the first resistor is

$$I = \frac{V}{R} = \frac{4.5\text{ V}}{468\ \Omega} = 9.6\text{ mA}$$

16. Problem

Two resistors are connected in **series**. Their resistances are $8\ \Omega$ and $4\ \Omega$. A difference in potential of 85 V is applied to the combination. What is the current through the $4\ \Omega$ resistor?

- a. 9.3 A
- b. 11 A
- c. 4.3 A
- d. 7.1 A

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 12\ \Omega$$

The current is the same through all components in series and its value is

$$I = \frac{V}{R} = \frac{85\text{ V}}{12\ \Omega} = 7.1\text{ A}$$

17. Problem

Two resistors are connected in **parallel**. Their resistances are $40\ \Omega$ and $39\ \Omega$. A battery applies 95 V to the combination. What is the current drawn from the battery?

- a. 3.2 A
- b. 3.7 A
- c. 4.8 A
- d. 2.7 A

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 19.7468354\ \Omega$$

The current drawn from the battery is

$$I = \frac{V}{R} = \frac{95 \text{ V}}{19.7468354 \Omega} = 4.8 \text{ A}$$

18. Problem

Three resistors are connected in **parallel**. Their resistances are 33Ω , 100Ω , and 57Ω . What is the equivalent resistance of the resistors?

- a. 25Ω
- b. 8.7Ω
- c. 17Ω
- d. 13Ω

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 17 \Omega$$

19. Problem

A 700 mA current flows into a parallel combination of a 27Ω and a 10Ω resistor. What current flows through the 27Ω resistor?

- a. 240 mA
- b. 190 mA
- c. 130 mA
- d. 95 mA

Solution

The total current is equal to the sum of the current through each resistor

$$I = I_1 + I_2$$

The voltage across each resistor is the same and $V = IR$ so

$$I_1 R_1 = I_2 R_2$$

Combining the two equations and solving for I_1 gives

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I = 190 \text{ mA}$$

20. Problem

When a battery with an emf of 6 V supplies a 8 A current, its terminal voltage is 4.8 V. What is the internal resistance of the battery?

- a. $0.17\ \Omega$
- b. $0.087\ \Omega$
- c. $0.21\ \Omega$
- d. $0.15\ \Omega$

Solution

The terminal resistance is related to the emf by $V_{terminal} = \mathcal{E} - Ir$. Therefore,

$$r = \frac{\mathcal{E} - V_{terminal}}{I} = 0.15\ \Omega$$