



# McRoberts Secondary

Circuits Unit Test 2025-12-17



## Personal Data

|              |         |
|--------------|---------|
| Family Name: |         |
| Given Name:  |         |
| Signature:   |         |
|              | checked |

## Registration Number

|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|

|   |                          |                          |                          |                          |                          |                          |                          |   |
|---|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|---|
| 0 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 0 |
| 1 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 1 |
| 2 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 2 |
| 3 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 3 |
| 4 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 4 |
| 5 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 5 |
| 6 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 6 |
| 7 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 7 |
| 8 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 8 |
| 9 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | 9 |

In this section **no** changes or modifications must be made!

Scrambling

0 0

Type

020

Exam ID(Physics 11)

25121700002

Please mark the boxes carefully: ☒ Not marked: ☐ or ☐

This document is scanned automatically. Please keep clean and do not bend or fold. For filling in the document please use a **blue or black pen**.

**Only clearly marked and positionally accurate crosses will be processed!**

## Answers 1 - 15

|    |                          |                          |                          |                          |
|----|--------------------------|--------------------------|--------------------------|--------------------------|
|    | a                        | b                        | c                        | d                        |
| 1  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 2  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 3  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 4  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 5  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 6  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 7  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 8  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 9  | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 10 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 11 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 12 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 13 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 14 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 15 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
|    | a                        | b                        | c                        | d                        |

## Answers 16 - 20

|    |                          |                          |                          |                          |
|----|--------------------------|--------------------------|--------------------------|--------------------------|
|    | a                        | b                        | c                        | d                        |
| 16 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 17 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 18 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 19 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
| 20 | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |
|    | a                        | b                        | c                        | d                        |





1. The current flowing in an electric circuit can be increased by
  - a. increasing voltage and decreasing resistance
  - b. decreasing voltage and increasing resistance
  - c. increasing voltage and increasing resistance
  - d. decreasing voltage and decreasing resistance
2. Car batteries are rated in “amp-hours”. This is a measure of their
  - a. energy density
  - b. power
  - c. energy capacity
  - d. electric charge
3. A battery is rated at 6.5 V and 5900 mAh. How much energy does the battery store at full charge?
  - a. 168 kJ
  - b. 140 kJ
  - c. 82.4 kJ
  - d. 263 kJ
4. What voltage is applied across a  $1.4\ \Omega$  resistor if the current is 1.9 A?
  - a. 1.4 V
  - b. 2.7 V
  - c. 5 V
  - d. 2.4 V
5. A lamp draws a current of 9.6 A when it is connected to a 2.5 V source. What is the resistance of the lamp?
  - a.  $3.8\ \Omega$
  - b.  $24\ \Omega$
  - c.  $0.26\ \Omega$
  - d.  $17\ \Omega$
6. A lamp with a resistance of  $6.8\ \Omega$  is placed across a potential difference of 8.5 V. What is the current through the lamp?
  - a. 22 A
  - b. 7.1 A
  - c. 0.8 A
  - d. 1.2 A
7. A voltage source of 3 V delivers a current of 9.5 A to an electric motor that is connected across its terminals. What power is consumed by the motor?
  - a. 46 W
  - b. 28 W
  - c. 25 W
  - d. 12 W

8. A space heater with a resistance of  $7.6\ \Omega$  operates at a voltage of  $117\text{ V}$ . How much energy does the space heater use in 3.2 hours?
- 6.7 kWh
  - 7.6 kWh
  - 5.8 kWh
  - 4.7 kWh
9. As more resistors are added in **series** to a constant voltage source, the power supplied by the source
- increases.
  - decreases.
  - remains the same.
  - not enough information.
10. Three resistors are connected in **series**. Their resistances are  $72\ \Omega$ ,  $21\ \Omega$ , and  $90\ \Omega$ . What is the equivalent resistance of the resistors?
- $180\ \Omega$
  - $14\ \Omega$
  - $96\ \Omega$
  - $48\ \Omega$
11. When different resistors are connected in series, it is true that
- the total resistance is equal to the greatest resistance of any individual resistor.
  - the power dissipated in each is the same.
  - the same current flows in each one.
  - the potential difference across each is the same.
12. You have a  $5\ \Omega$  light bulb and a  $10\ \Omega$  light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?
- The  $5\ \Omega$  bulb is brighter.
  - The  $10\ \Omega$  bulb is brighter.
  - Both bulbs glow at the same brightness.
  - It depends on the voltage.
13. A total of 856 resistors, all with resistance  $719\ \Omega$ , are connected in **parallel**. What is the equivalent resistance of the resistors?
- $0.53\ \Omega$
  - $0.84\ \Omega$
  - $1.3\ \Omega$
  - $0.62\ \Omega$
14. A total of 280 Christmas light bulbs, all with resistance  $906\ \Omega$ , are connected in **series**. What is the equivalent resistance of the lights?
- $370\text{ k}\Omega$
  - $190\text{ k}\Omega$
  - $250\text{ k}\Omega$
  - $160\text{ k}\Omega$

15. Two resistors are connected in **parallel**. Their resistances are  $202\ \Omega$  and  $406\ \Omega$ . A battery applies  $6.3\text{ V}$  to the combination. What is the current through the  $202\ \Omega$  resistor?
- $40\text{ mA}$
  - $31\text{ mA}$
  - $26\text{ mA}$
  - $43\text{ mA}$
16. Two resistors are connected in **series**. Their resistances are  $7\ \Omega$  and  $10\ \Omega$ . A difference in potential of  $56\text{ V}$  is applied to the combination. What is the current through the  $10\ \Omega$  resistor?
- $2.2\text{ A}$
  - $2.7\text{ A}$
  - $4.3\text{ A}$
  - $3.3\text{ A}$
17. Two resistors are connected in **parallel**. Their resistances are  $24\ \Omega$  and  $21\ \Omega$ . A battery applies  $14\text{ V}$  to the combination. What is the current drawn from the battery?
- $0.85\text{ A}$
  - $1.6\text{ A}$
  - $1.4\text{ A}$
  - $1.2\text{ A}$
18. Three resistors are connected in **parallel**. Their resistances are  $92\ \Omega$ ,  $2\ \Omega$ , and  $72\ \Omega$ . What is the equivalent resistance of the resistors?
- $1.9\ \Omega$
  - $2.5\ \Omega$
  - $3.5\ \Omega$
  - $2.8\ \Omega$
19. A  $200\text{ mA}$  current flows into a parallel combination of a  $29\ \Omega$  and a  $14\ \Omega$  resistor. What current flows through the  $29\ \Omega$  resistor?
- $57\text{ mA}$
  - $86\text{ mA}$
  - $93\text{ mA}$
  - $65\text{ mA}$
20. When a battery with an emf of  $1.8\text{ V}$  supplies a  $1.2\text{ A}$  current, its terminal voltage is  $1.5\text{ V}$ . What is the internal resistance of the battery?
- $0.22\ \Omega$
  - $0.18\ \Omega$
  - $0.46\ \Omega$
  - $0.25\ \Omega$