

Physics 11

Circuits Unit Test Solutions

- | | | | | | | | |
|--------|-------------------------------------|----|-------------------------------------|----|-------------------------------------|----|-------------------------------------|
| 1. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 2. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 3. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 4. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 5. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 6. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 7. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 8. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 9. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 10. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 11. a. | <input checked="" type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 12. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 13. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 14. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 15. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 16. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input checked="" type="checkbox"/> | d. | <input type="checkbox"/> |
| 17. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 18. a. | <input type="checkbox"/> | b. | <input checked="" type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input type="checkbox"/> |
| 19. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |
| 20. a. | <input type="checkbox"/> | b. | <input type="checkbox"/> | c. | <input type="checkbox"/> | d. | <input checked="" type="checkbox"/> |

1. Problem

Which device can be used to measure the current in a circuit?

- a. ammeter
- b. voltmeter
- c. potentiometer
- d. ohmmeter

Solution

Current can be measured by an ammeter.

2. Problem

Car batteries are rated in “amp-hours”. This is a measure of their

- a. power
- b. energy capacity
- c. electric charge
- d. current

Solution

The amp-hour comes from multiplying current and time and is therefore a unit of electric charge.

3. Problem

A battery is rated at 4.8 V and 2300 mAh. How much energy does the battery store at full charge?

- a. 66.8 kJ
- b. 40 kJ
- c. 79.2 kJ
- d. 60.3 kJ

Solution

Convert to SI units and multiply the voltage by the charge:

$$E = QV = (2300 \text{ mAh} \times 3.6 \text{ C/mAh})(4.8 \text{ V}) = 40 \text{ kJ}$$

4. Problem

What voltage is applied across a 7.3Ω resistor if the current is 7.6 A?

- a. 55 V
- b. 1 V
- c. 14 V
- d. 30 V

Solution

Use Ohm's law:

$$V = IR = (7.6 \text{ A})(7.3 \Omega) = 55 \text{ V}$$

5. Problem

A lamp draws a current of 7.2 A when it is connected to a 5.2 V source. What is the resistance of the lamp?

- a. $5.6\ \Omega$
- b. $0.72\ \Omega$
- c. $20\ \Omega$
- d. $37\ \Omega$

Solution

Use Ohm's law:

$$R = \frac{V}{I} = \frac{5.2\text{ V}}{7.2\text{ A}} = 0.72\ \Omega$$

6. Problem

A lamp with a resistance of $6.8\ \Omega$ is placed across a potential difference of 8.5 V. What is the current through the lamp?

- a. 0.8 A
- b. 0.94 A
- c. 1.2 A
- d. 58 A

Solution

Use Ohm's law:

$$I = \frac{V}{R} = \frac{8.5\text{ V}}{6.8\ \Omega} = 1.2\text{ A}$$

7. Problem

A voltage source of 9.5 V delivers a current of 8 A to an electric motor that is connected across its terminals. What power is consumed by the motor?

- a. 68 W
- b. 1.2 W
- c. 76 W
- d. 58 W

Solution

Use the formula for the power in a circuit:

$$P = IV = (8\text{ A})(9.5\text{ V}) = 76\text{ W}$$

8. Problem

A space heater with a resistance of $5.4\ \Omega$ operates at a voltage of 116 V . How much energy does the space heater use in 8.1 hours?

- a. 20 kWh
- b. 18 kWh
- c. 13 kWh
- d. 16 kWh

Solution

Find the power of the device using $P = IV = V^2/R$ and multiply by the time. Remember to convert all units.

$$E = Pt = \frac{V^2}{R}t = \frac{(116\text{ V})^2}{5.4\ \Omega}(8.1\text{ h}) = 20000\text{ Wh} = 20\text{ kWh}$$

9. Problem

As more resistors are added in **series** to a constant voltage source, the power supplied by the source

- a. increases.
- b. decreases.
- c. remains the same.
- d. not enough information.

Solution

The total resistance increases, causing the total current to decrease. Since the voltage is constant and $P = IV$, the power decreases.

10. Problem

Three resistors are connected in **series**. Their resistances are $71\ \Omega$, $95\ \Omega$, and $86\ \Omega$. What is the equivalent resistance of the resistors?

- a. $110\ \Omega$
- b. $410\ \Omega$
- c. $370\ \Omega$
- d. $250\ \Omega$

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 252\ \Omega$$

11. Problem

When different resistors are connected in series, it is true that

- a. the same current flows in each one.
- b. the total resistance is equal to the greatest resistance of any individual resistor.
- c. the potential difference across each is the same.
- d. the power dissipated in each is the same.

Solution

The current is the same in resistors in series.

12. Problem

You have a $5\ \Omega$ light bulb and a $10\ \Omega$ light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?

- a. The $5\ \Omega$ bulb is brighter.
- b. The $10\ \Omega$ bulb is brighter.
- c. Both bulbs glow at the same brightness.
- d. It depends on the voltage.

Solution

The current through both bulbs is the same since they are placed in series. However, the voltage drop is greater for the greater resistance. Since $P = IV$, and V is greater for the greater resistance, the $10\ \Omega$ light bulb is brighter.

13. Problem

A total of 713 resistors, all with resistance $277\ \Omega$, are connected in **parallel**. What is the equivalent resistance of the resistors?

- a. $0.3\ \Omega$
- b. $0.24\ \Omega$
- c. $0.39\ \Omega$
- d. $0.49\ \Omega$

Solution

The equivalent resistance of resistors in parallel when they all have the same resistance R_i is

$$R = \left(\frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_i} + \dots \right)^{-1} = \frac{R_i}{713} = 0.39\ \Omega$$

14. Problem

A total of 654 Christmas light bulbs, all with resistance $350\ \Omega$, are connected in **series**. What is the equivalent resistance of the lights?

- a. $190\ \text{k}\Omega$
- b. $160\ \text{k}\Omega$
- c. $130\ \text{k}\Omega$
- d. $230\ \text{k}\Omega$

Solution

The equivalent resistance of resistors in series when they all have the same resistance R_i is

$$R = R_i + R_i + R_i + \dots + R_i = 654R_i = 230\ \text{k}\Omega$$

15. Problem

Two resistors are connected in **parallel**. Their resistances are $441\ \Omega$ and $335\ \Omega$. A battery applies $6.6\ \text{V}$ to the combination. What is the current through the $441\ \Omega$ resistor?

- a. $13\ \text{mA}$
- b. $15\ \text{mA}$
- c. $22\ \text{mA}$
- d. $26\ \text{mA}$

Solution

The full voltage of the battery is applied to both resistors. The current through the first resistor is

$$I = \frac{V}{R} = \frac{6.6\ \text{V}}{441\ \Omega} = 15\ \text{mA}$$

16. Problem

Two resistors are connected in **series**. Their resistances are $6\ \Omega$ and $8\ \Omega$. A difference in potential of $73\ \text{V}$ is applied to the combination. What is the current through the $8\ \Omega$ resistor?

- a. $6.3\ \text{A}$
- b. $5.8\ \text{A}$
- c. $5.2\ \text{A}$
- d. $7.9\ \text{A}$

Solution

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 14\ \Omega$$

The current is the same through all components in series and its value is

$$I = \frac{V}{R} = \frac{73\ \text{V}}{14\ \Omega} = 5.2\ \text{A}$$

17. Problem

Two resistors are connected in **parallel**. Their resistances are $18\ \Omega$ and $39\ \Omega$. A battery applies $39\ \text{V}$ to the combination. What is the current drawn from the battery?

- a. $5.6\ \text{A}$
- b. $2.1\ \text{A}$
- c. $4.7\ \text{A}$
- d. $3.2\ \text{A}$

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 12.3157895\ \Omega$$

The current drawn from the battery is

$$I = \frac{V}{R} = \frac{39 \text{ V}}{12.3157895 \Omega} = 3.2 \text{ A}$$

18. Problem

Three resistors are connected in **parallel**. Their resistances are 39Ω , 74Ω , and 64Ω . What is the equivalent resistance of the resistors?

- a. 12Ω
- b. 18Ω
- c. 16Ω
- d. 14Ω

Solution

The equivalent resistance of resistors in parallel is

$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 18 \Omega$$

19. Problem

A 800 mA current flows into a parallel combination of a 44Ω and a 50Ω resistor. What current flows through the 44Ω resistor?

- a. 850 mA
- b. 680 mA
- c. 580 mA
- d. 430 mA

Solution

The total current is equal to the sum of the current through each resistor

$$I = I_1 + I_2$$

The voltage across each resistor is the same and $V = IR$ so

$$I_1 R_1 = I_2 R_2$$

Combining the two equations and solving for I_1 gives

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I = 430 \text{ mA}$$

20. Problem

When a battery with an emf of 5 V supplies a 9.8 A current, its terminal voltage is 4.4 V. What is the internal resistance of the battery?

- a. $0.047\ \Omega$
- b. $0.033\ \Omega$
- c. $0.055\ \Omega$
- d. $0.061\ \Omega$

Solution

The terminal resistance is related to the emf by $V_{\text{terminal}} = \mathcal{E} - Ir$. Therefore,

$$r = \frac{\mathcal{E} - V_{\text{terminal}}}{I} = 0.061\ \Omega$$