



# McRoberts Secondary

Circuits Unit Retest 2025-01-21



## Personal Data

Family Name:
Given Name:
Signature:
checked

## Registration Number

--	--	--	--	--	--	--	--

0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	0
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	1
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	2
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	3
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	4
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	5
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	6
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	7
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	8
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	9

In this section **no** changes or modifications must be made!

Scrambling

0 0

Type

020

Exam ID(Physics 11)

25012100002

Please mark the boxes carefully: ☒ Not marked: ☐ or ☐

This document is scanned automatically. Please keep clean and do not bend or fold. For filling in the document please use a **blue or black pen**.

**Only clearly marked and positionally accurate crosses will be processed!**

## Answers 1 - 15

	a	b	c	d
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
11	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
12	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
13	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
14	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
15	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	a	b	c	d

## Answers 16 - 20

	a	b	c	d
16	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
17	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
18	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
19	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
20	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	a	b	c	d





1. The current flowing in an electric circuit can be increased by
  - a. increasing voltage and decreasing resistance
  - b. decreasing voltage and increasing resistance
  - c. increasing voltage and increasing resistance
  - d. decreasing voltage and decreasing resistance
2. An ammeter is connected in \_\_\_\_\_ and a voltmeter is connected in \_\_\_\_\_.
  - a. series, series
  - b. series, parallel
  - c. parallel, series
  - d. parallel, parallel
3. A battery is rated at 10 V and 5600 mAh. How much energy does the battery store at full charge?
  - a. 105 kJ
  - b. 174 kJ
  - c. 346 kJ
  - d. 200 kJ
4. What voltage is applied across a  $3.6\ \Omega$  resistor if the current is 5.9 A?
  - a. 21 V
  - b. 19 V
  - c. 1.6 V
  - d. 12 V
5. A lamp draws a current of 9.7 A when it is connected to a 4.9 V source. What is the resistance of the lamp?
  - a.  $0.51\ \Omega$
  - b.  $2\ \Omega$
  - c.  $0.39\ \Omega$
  - d.  $0.27\ \Omega$
6. A lamp with a resistance of  $6.8\ \Omega$  is placed across a potential difference of 8.5 V. What is the current through the lamp?
  - a. 17 A
  - b. 58 A
  - c. 0.68 A
  - d. 1.2 A
7. A voltage source of 6.4 V delivers a current of 2.1 A to an electric motor that is connected across its terminals. What power is consumed by the motor?
  - a. 3 W
  - b. 11 W
  - c. 16 W
  - d. 13 W

8. An electronic device is powered by a 3.5 V battery. The current used to operate the device is 200 mA. How much energy does the device use in 6 minutes?
- 4200 J
  - 4.2 J
  - 250 J
  - 140 J
9. As more resistors are added in **series** to a constant voltage source, the power supplied by the source
- increases.
  - decreases.
  - remains the same.
  - not enough information.
10. Three resistors are connected in **series**. Their resistances are  $82\ \Omega$ ,  $42\ \Omega$ , and  $28\ \Omega$ . What is the equivalent resistance of the resistors?
- $150\ \Omega$
  - $53\ \Omega$
  - $170\ \Omega$
  - $270\ \Omega$
11. When different resistors are connected in parallel, it is true that
- the same current flows in each one.
  - their equivalent resistance is greater than the resistance of one of the resistors.
  - the power dissipated in each is the same.
  - the potential difference across each is the same.
12. You have a 60 W light bulb and a 100 W light bulb. Instead of connecting them the normal way, you make a circuit that places them in series across the normal household voltage. Which statement is correct?
- Both bulbs glow at the same reduced brightness.
  - Both bulbs glow at the same increased brightness.
  - The 100 W bulb glows brighter than the 60 W bulb.
  - The 60 W bulb glows brighter than the 100 W bulb.
13. A total of 799 resistors, all with resistance  $569\ \Omega$ , are connected in **parallel**. What is the equivalent resistance of the resistors?
- $0.46\ \Omega$
  - $0.71\ \Omega$
  - $0.62\ \Omega$
  - $0.36\ \Omega$
14. A total of 703 Christmas light bulbs, all with resistance  $0.628\ \Omega$ , are connected in **series**. What is the equivalent resistance of the lights?
- $620\ \Omega$
  - $490\ \Omega$
  - $540\ \Omega$
  - $440\ \Omega$

15. Two resistors are connected in **parallel**. Their resistances are  $347\ \Omega$  and  $323\ \Omega$ . A battery applies  $1.7\ \text{V}$  to the combination. What is the current through the  $347\ \Omega$  resistor?
- $4.9\ \text{mA}$
  - $4.2\ \text{mA}$
  - $8.4\ \text{mA}$
  - $3.5\ \text{mA}$
16. Two resistors are connected in **series**. Their resistances are  $4\ \Omega$  and  $3\ \Omega$ . A difference in potential of  $68\ \text{V}$  is applied to the combination. What is the current through the  $3\ \Omega$  resistor?
- $9.7\ \text{A}$
  - $5.3\ \text{A}$
  - $7\ \text{A}$
  - $8.5\ \text{A}$
17. Two resistors are connected in **parallel**. Their resistances are  $16\ \Omega$  and  $18\ \Omega$ . A battery applies  $56\ \text{V}$  to the combination. What is the current drawn from the battery?
- $11\ \text{A}$
  - $6.6\ \text{A}$
  - $9.1\ \text{A}$
  - $3.7\ \text{A}$
18. Three resistors are connected in **parallel**. Their resistances are  $78\ \Omega$ ,  $45\ \Omega$ , and  $70\ \Omega$ . What is the equivalent resistance of the resistors?
- $15\ \Omega$
  - $20\ \Omega$
  - $18\ \Omega$
  - $40\ \Omega$
19. A  $800\ \text{mA}$  current flows into a parallel combination of a  $82\ \Omega$  and a  $48\ \Omega$  resistor. What current flows through the  $82\ \Omega$  resistor?
- $170\ \text{mA}$
  - $460\ \text{mA}$
  - $300\ \text{mA}$
  - $240\ \text{mA}$
20. When a battery with an emf of  $7\ \text{V}$  supplies a  $0.31\ \text{A}$  current, its terminal voltage is  $5.9\ \text{V}$ . What is the internal resistance of the battery?
- $3.1\ \Omega$
  - $3.5\ \Omega$
  - $2.4\ \Omega$
  - $5.3\ \Omega$