



# McRoberts Secondary

Circuits Unit Retest 2025-01-21



## Personal Data

Family Name:
Given Name:
Signature:
checked

## Registration Number

--	--	--	--	--	--	--	--

0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	0
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	1
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	2
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	3
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	4
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	5
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	6
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	7
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	8
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	9

In this section **no** changes or modifications must be made!

Scrambling

0 0

Type

020

Exam ID(Physics 11)

25012100001

Please mark the boxes carefully: ☒ Not marked: ☐ or ☐

This document is scanned automatically. Please keep clean and do not bend or fold. For filling in the document please use a **blue or black pen**.

**Only clearly marked and positionally accurate crosses will be processed!**

## Answers 1 - 15

	a	b	c	d
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
11	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
12	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
13	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
14	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
15	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

## Answers 16 - 20

	a	b	c	d
16	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
17	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
18	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
19	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
20	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

a b c d

a b c d





1. The current flowing in an electric circuit can be increased by
  - a. increasing voltage and decreasing resistance
  - b. decreasing voltage and increasing resistance
  - c. increasing voltage and increasing resistance
  - d. decreasing voltage and decreasing resistance
2. An ammeter is connected in \_\_\_\_\_ and a voltmeter is connected in \_\_\_\_\_.
  - a. series, series
  - b. series, parallel
  - c. parallel, series
  - d. parallel, parallel
3. A battery is rated at 3.7 V and 2100 mAh. How much energy does the battery store at full charge?
  - a. 14.7 kJ
  - b. 22.4 kJ
  - c. 28 kJ
  - d. 31.2 kJ
4. What voltage is applied across a  $2.7\ \Omega$  resistor if the current is 5.8 A?
  - a. 4.8 V
  - b. 13 V
  - c. 0.44 V
  - d. 16 V
5. A lamp draws a current of 8.5 A when it is connected to a 6.4 V source. What is the resistance of the lamp?
  - a.  $1.3\ \Omega$
  - b.  $0.75\ \Omega$
  - c.  $0.67\ \Omega$
  - d.  $54\ \Omega$
6. A lamp with a resistance of  $6.8\ \Omega$  is placed across a potential difference of 8.5 V. What is the current through the lamp?
  - a. 30 A
  - b. 0.8 A
  - c. 58 A
  - d. 1.2 A
7. A voltage source of 6.1 V delivers a current of 6.2 A to an electric motor that is connected across its terminals. What power is consumed by the motor?
  - a. 66 W
  - b. 0.98 W
  - c. 62 W
  - d. 38 W

8. An electronic device is powered by a 4.4 V battery. The current used to operate the device is 190 mA. How much energy does the device use in 9.4 minutes?
- 7.9 J
  - 470 J
  - 110 J
  - 7900 J
9. As more resistors are added in **series** to a constant voltage source, the power supplied by the source
- increases.
  - decreases.
  - remains the same.
  - not enough information.
10. Three resistors are connected in **series**. Their resistances are  $33\ \Omega$ ,  $66\ \Omega$ , and  $78\ \Omega$ . What is the equivalent resistance of the resistors?
- $95\ \Omega$
  - $160\ \Omega$
  - $220\ \Omega$
  - $180\ \Omega$
11. When different resistors are connected in parallel, it is true that
- the power dissipated in each is the same.
  - the potential difference across each is the same.
  - their equivalent resistance is greater than the resistance of one of the resistors.
  - the same current flows in each one.
12. You have a 60 W light bulb and a 100 W light bulb. Instead of connecting them the normal way, you make a circuit that places them in series across the normal household voltage. Which statement is correct?
- Both bulbs glow at the same reduced brightness.
  - Both bulbs glow at the same increased brightness.
  - The 100 W bulb glows brighter than the 60 W bulb.
  - The 60 W bulb glows brighter than the 100 W bulb.
13. A total of 495 resistors, all with resistance  $147\ \Omega$ , are connected in **parallel**. What is the equivalent resistance of the resistors?
- $0.3\ \Omega$
  - $0.38\ \Omega$
  - $0.41\ \Omega$
  - $0.34\ \Omega$
14. A total of 169 Christmas light bulbs, all with resistance  $0.52\ \Omega$ , are connected in **series**. What is the equivalent resistance of the lights?
- $88\ \Omega$
  - $110\ \Omega$
  - $120\ \Omega$
  - $50\ \Omega$

15. Two resistors are connected in **parallel**. Their resistances are  $220\ \Omega$  and  $415\ \Omega$ . A battery applies  $4.2\text{ V}$  to the combination. What is the current through the  $220\ \Omega$  resistor?
- $16\text{ mA}$
  - $19\text{ mA}$
  - $14\text{ mA}$
  - $12\text{ mA}$
16. Two resistors are connected in **series**. Their resistances are  $4\ \Omega$  and  $1\ \Omega$ . A difference in potential of  $18\text{ V}$  is applied to the combination. What is the current through the  $1\ \Omega$  resistor?
- $2.8\text{ A}$
  - $2.4\text{ A}$
  - $3.6\text{ A}$
  - $3.2\text{ A}$
17. Two resistors are connected in **parallel**. Their resistances are  $36\ \Omega$  and  $37\ \Omega$ . A battery applies  $16\text{ V}$  to the combination. What is the current drawn from the battery?
- $1.6\text{ A}$
  - $1.2\text{ A}$
  - $0.88\text{ A}$
  - $1\text{ A}$
18. Three resistors are connected in **parallel**. Their resistances are  $52\ \Omega$ ,  $61\ \Omega$ , and  $79\ \Omega$ . What is the equivalent resistance of the resistors?
- $14\ \Omega$
  - $19\ \Omega$
  - $21\ \Omega$
  - $16\ \Omega$
19. A  $400\text{ mA}$  current flows into a parallel combination of a  $93\ \Omega$  and a  $71\ \Omega$  resistor. What current flows through the  $93\ \Omega$  resistor?
- $150\text{ mA}$
  - $170\text{ mA}$
  - $140\text{ mA}$
  - $310\text{ mA}$
20. When a battery with an emf of  $2.5\text{ V}$  supplies a  $0.39\text{ A}$  current, its terminal voltage is  $1.2\text{ V}$ . What is the internal resistance of the battery?
- $2.5\ \Omega$
  - $6.5\ \Omega$
  - $4.2\ \Omega$
  - $3.3\ \Omega$