

# Physics 11

## Circuits Unit Test Solutions

1. a. ☒ b. ☐ c. ☐ d. ☐
2. a. ☐ b. ☐ c. ☐ d. ☒
3. a. ☐ b. ☒ c. ☐ d. ☐
4. a. ☐ b. ☒ c. ☐ d. ☐
5. a. ☐ b. ☐ c. ☒ d. ☐
6. a. ☐ b. ☐ c. ☐ d. ☒
7. a. ☐ b. ☒ c. ☐ d. ☐
8. a. ☐ b. ☐ c. ☒ d. ☐
9. a. ☐ b. ☒ c. ☐ d. ☐
10. a. ☒ b. ☐ c. ☐ d. ☐
11. a. ☐ b. ☐ c. ☒ d. ☐
12. a. ☐ b. ☒ c. ☐ d. ☐
13. a. ☐ b. ☒ c. ☐ d. ☐
14. a. ☐ b. ☐ c. ☒ d. ☐
15. a. ☐ b. ☒ c. ☐ d. ☐
16. a. ☐ b. ☐ c. ☐ d. ☒
17. a. ☐ b. ☐ c. ☐ d. ☒
18. a. ☒ b. ☐ c. ☐ d. ☐
19. a. ☐ b. ☐ c. ☐ d. ☒
20. a. ☐ b. ☐ c. ☐ d. ☒

**1. Problem**

The current flowing in an electric circuit can be increased by

- a. increasing voltage and decreasing resistance
- b. decreasing voltage and increasing resistance
- c. increasing voltage and increasing resistance
- d. decreasing voltage and decreasing resistance

**Solution**

Ohm's law states that

$$I = \frac{V}{R}$$

Therefore, current can be increased by increasing voltage and decreasing resistance.

**2. Problem**

Car batteries are rated in "amp-hours". This is a measure of their

- a. energy density
- b. power
- c. energy capacity
- d. electric charge

**Solution**

The amp-hour comes from multiplying current and time and is therefore a unit of electric charge.

**3. Problem**

A battery is rated at 6.5 V and 5900 mAh. How much energy does the battery store at full charge?

- a. 168 kJ
- b. 140 kJ
- c. 82.4 kJ
- d. 263 kJ

**Solution**

Convert to SI units and multiply the voltage by the charge:

$$E = QV = (5900 \text{ mAh} \times 3.6 \text{ C/mAh})(6.5 \text{ V}) = 140 \text{ kJ}$$

**4. Problem**

What voltage is applied across a  $1.4 \Omega$  resistor if the current is 1.9 A?

- a. 1.4 V
- b. 2.7 V
- c. 5 V
- d. 2.4 V

**Solution**

Use Ohm's law:

$$V = IR = (1.9\text{ A})(1.4\Omega) = 2.7\text{ V}$$

**5. Problem**

A lamp draws a current of 9.6 A when it is connected to a 2.5 V source. What is the resistance of the lamp?

- a.  $3.8\Omega$
- b.  $24\Omega$
- c.  $0.26\Omega$
- d.  $17\Omega$

**Solution**

Use Ohm's law:

$$R = \frac{V}{I} = \frac{2.5\text{ V}}{9.6\text{ A}} = 0.26\Omega$$

**6. Problem**

A lamp with a resistance of  $6.8\Omega$  is placed across a potential difference of 8.5 V. What is the current through the lamp?

- a. 22 A
- b. 7.1 A
- c. 0.8 A
- d. 1.2 A

**Solution**

Use Ohm's law:

$$I = \frac{V}{R} = \frac{8.5\text{ V}}{6.8\Omega} = 1.2\text{ A}$$

**7. Problem**

A voltage source of 3 V delivers a current of 9.5 A to an electric motor that is connected across its terminals. What power is consumed by the motor?

- a. 46 W
- b. 28 W
- c. 25 W
- d. 12 W

**Solution**

Use the formula for the power in a circuit:

$$P = IV = (9.5\text{ A})(3\text{ V}) = 28\text{ W}$$

**8. Problem**

A space heater with a resistance of  $7.6\ \Omega$  operates at a voltage of  $117\text{ V}$ . How much energy does the space heater use in 3.2 hours?

- a. 6.7 kWh
- b. 7.6 kWh
- c. 5.8 kWh
- d. 4.7 kWh

**Solution**

Find the power of the device using  $P = IV = V^2/R$  and multiply by the time. Remember to convert all units.

$$E = Pt = \frac{V^2}{R}t = \frac{(117\text{ V})^2}{7.6\ \Omega}(3.2\text{ h}) = 5800\text{ Wh} = 5.8\text{ kWh}$$

**9. Problem**

As more resistors are added in **series** to a constant voltage source, the power supplied by the source

- a. increases.
- b. decreases.
- c. remains the same.
- d. not enough information.

**Solution**

The total resistance increases, causing the total current to decrease. Since the voltage is constant and  $P = IV$ , the power decreases.

**10. Problem**

Three resistors are connected in **series**. Their resistances are  $72\ \Omega$ ,  $21\ \Omega$ , and  $90\ \Omega$ . What is the equivalent resistance of the resistors?

- a.  $180\ \Omega$
- b.  $14\ \Omega$
- c.  $96\ \Omega$
- d.  $48\ \Omega$

**Solution**

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 183\ \Omega$$

**11. Problem**

When different resistors are connected in series, it is true that

- a. the total resistance is equal to the greatest resistance of any individual resistor.
- b. the power dissipated in each is the same.
- c. the same current flows in each one.
- d. the potential difference across each is the same.

**Solution**

The current is the same in resistors in series.

**12. Problem**

You have a  $5\ \Omega$  light bulb and a  $10\ \Omega$  light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?

- a. The  $5\ \Omega$  bulb is brighter.
- b. The  $10\ \Omega$  bulb is brighter.
- c. Both bulbs glow at the same brightness.
- d. It depends on the voltage.

**Solution**

The current through both bulbs is the same since they are placed in series. However, the voltage drop is greater for the greater resistance. Since  $P = IV$ , and  $V$  is greater for the greater resistance, the  $10\ \Omega$  light bulb is brighter.

**13. Problem**

A total of 856 resistors, all with resistance  $719\ \Omega$ , are connected in **parallel**. What is the equivalent resistance of the resistors?

- a.  $0.53\ \Omega$
- b.  $0.84\ \Omega$
- c.  $1.3\ \Omega$
- d.  $0.62\ \Omega$

**Solution**

The equivalent resistance of resistors in parallel when they all have the same resistance  $R_i$  is

$$R = \left( \frac{1}{R_i} + \frac{1}{R_i} + \frac{1}{R_i} + \dots \right)^{-1} = \frac{R_i}{856} = 0.84\ \Omega$$

**14. Problem**

A total of 280 Christmas light bulbs, all with resistance  $906\ \Omega$ , are connected in **series**. What is the equivalent resistance of the lights?

- a.  $370\ \text{k}\Omega$
- b.  $190\ \text{k}\Omega$
- c.  $250\ \text{k}\Omega$
- d.  $160\ \text{k}\Omega$

**Solution**

The equivalent resistance of resistors in series when they all have the same resistance  $R_i$  is

$$R = R_i + R_i + R_i + \dots + R_i = 280R_i = 250\ \text{k}\Omega$$

**15. Problem**

Two resistors are connected in **parallel**. Their resistances are  $202\ \Omega$  and  $406\ \Omega$ . A battery applies  $6.3\ \text{V}$  to the combination. What is the current through the  $202\ \Omega$  resistor?

- a.  $40\ \text{mA}$
- b.  $31\ \text{mA}$
- c.  $26\ \text{mA}$
- d.  $43\ \text{mA}$

**Solution**

The full voltage of the battery is applied to both resistors. The current through the first resistor is

$$I = \frac{V}{R} = \frac{6.3\ \text{V}}{202\ \Omega} = 31\ \text{mA}$$

**16. Problem**

Two resistors are connected in **series**. Their resistances are  $7\ \Omega$  and  $10\ \Omega$ . A difference in potential of  $56\ \text{V}$  is applied to the combination. What is the current through the  $10\ \Omega$  resistor?

- a.  $2.2\ \text{A}$
- b.  $2.7\ \text{A}$
- c.  $4.3\ \text{A}$
- d.  $3.3\ \text{A}$

**Solution**

The equivalent resistance of resistors in series is the sum of the resistances.

$$R = R_1 + R_2 + R_3 = 17\ \Omega$$

The current is the same through all components in series and its value is

$$I = \frac{V}{R} = \frac{56\ \text{V}}{17\ \Omega} = 3.3\ \text{A}$$

**17. Problem**

Two resistors are connected in **parallel**. Their resistances are  $24\ \Omega$  and  $21\ \Omega$ . A battery applies  $14\ \text{V}$  to the combination. What is the current drawn from the battery?

- a.  $0.85\ \text{A}$
- b.  $1.6\ \text{A}$
- c.  $1.4\ \text{A}$
- d.  $1.2\ \text{A}$

**Solution**

The equivalent resistance of resistors in parallel is

$$R = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 11.2\ \Omega$$

The current drawn from the battery is

$$I = \frac{V}{R} = \frac{14\text{ V}}{11.2\ \Omega} = 1.2\text{ A}$$

**18. Problem**

Three resistors are connected in **parallel**. Their resistances are  $92\ \Omega$ ,  $2\ \Omega$ , and  $72\ \Omega$ . What is the equivalent resistance of the resistors?

- a.  $1.9\ \Omega$
- b.  $2.5\ \Omega$
- c.  $3.5\ \Omega$
- d.  $2.8\ \Omega$

**Solution**

The equivalent resistance of resistors in parallel is

$$R = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 1.9\ \Omega$$

**19. Problem**

A  $200\text{ mA}$  current flows into a parallel combination of a  $29\ \Omega$  and a  $14\ \Omega$  resistor. What current flows through the  $29\ \Omega$  resistor?

- a.  $57\text{ mA}$
- b.  $86\text{ mA}$
- c.  $93\text{ mA}$
- d.  $65\text{ mA}$

**Solution**

The total current is equal to the sum of the current through each resistor

$$I = I_1 + I_2$$

The voltage across each resistor is the same and  $V = IR$  so

$$I_1 R_1 = I_2 R_2$$

Combining the two equations and solving for  $I_1$  gives

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I = 65\text{ mA}$$

**20. Problem**

When a battery with an emf of 1.8 V supplies a 1.2 A current, its terminal voltage is 1.5 V. What is the internal resistance of the battery?

- a.  $0.22\ \Omega$
- b.  $0.18\ \Omega$
- c.  $0.46\ \Omega$
- d.  $0.25\ \Omega$

**Solution**

The terminal resistance is related to the emf by  $V_{\text{terminal}} = \mathcal{E} - Ir$ . Therefore,

$$r = \frac{\mathcal{E} - V_{\text{terminal}}}{I} = 0.25\ \Omega$$