



# McRoberts Secondary

Circuits Unit Test 2025-12-17



## Personal Data

Family Name:
Given Name:
Signature:
checked

## Registration Number

--	--	--	--	--	--	--	--

0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	0
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	1
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	2
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	3
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	4
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	5
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	6
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	7
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	8
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	9

In this section **no** changes or modifications must be made!

Scrambling

0 0

Type

020

Exam ID(Physics 11)

25121700001

Please mark the boxes carefully: ☒ Not marked: ☐ or ☐

This document is scanned automatically. Please keep clean and do not bend or fold. For filling in the document please use a **blue or black pen**.

**Only clearly marked and positionally accurate crosses will be processed!**

## Answers 1 - 15

	a	b	c	d
1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
2	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
3	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
4	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
5	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
6	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
7	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
8	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
9	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
10	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
11	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
12	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
13	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
14	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
15	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	a	b	c	d

## Answers 16 - 20

	a	b	c	d
16	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
17	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
18	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
19	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
20	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	a	b	c	d





1. Which device can be used to measure the current in a circuit?
  - a. ammeter
  - b. voltmeter
  - c. potentiometer
  - d. ohmmeter
2. Car batteries are rated in "amp-hours". This is a measure of their
  - a. power
  - b. energy capacity
  - c. electric charge
  - d. current
3. A battery is rated at 4.8 V and 2300 mAh. How much energy does the battery store at full charge?
  - a. 66.8 kJ
  - b. 40 kJ
  - c. 79.2 kJ
  - d. 60.3 kJ
4. What voltage is applied across a  $7.3\ \Omega$  resistor if the current is 7.6 A?
  - a. 55 V
  - b. 1 V
  - c. 14 V
  - d. 30 V
5. A lamp draws a current of 7.2 A when it is connected to a 5.2 V source. What is the resistance of the lamp?
  - a.  $5.6\ \Omega$
  - b.  $0.72\ \Omega$
  - c.  $20\ \Omega$
  - d.  $37\ \Omega$
6. A lamp with a resistance of  $6.8\ \Omega$  is placed across a potential difference of 8.5 V. What is the current through the lamp?
  - a. 0.8 A
  - b. 0.94 A
  - c. 1.2 A
  - d. 58 A
7. A voltage source of 9.5 V delivers a current of 8 A to an electric motor that is connected across its terminals. What power is consumed by the motor?
  - a. 68 W
  - b. 1.2 W
  - c. 76 W
  - d. 58 W

8. A space heater with a resistance of  $5.4\ \Omega$  operates at a voltage of  $116\text{ V}$ . How much energy does the space heater use in 8.1 hours?
- 20 kWh
  - 18 kWh
  - 13 kWh
  - 16 kWh
9. As more resistors are added in **series** to a constant voltage source, the power supplied by the source
- increases.
  - decreases.
  - remains the same.
  - not enough information.
10. Three resistors are connected in **series**. Their resistances are  $71\ \Omega$ ,  $95\ \Omega$ , and  $86\ \Omega$ . What is the equivalent resistance of the resistors?
- $110\ \Omega$
  - $410\ \Omega$
  - $370\ \Omega$
  - $250\ \Omega$
11. When different resistors are connected in series, it is true that
- the same current flows in each one.
  - the total resistance is equal to the greatest resistance of any individual resistor.
  - the potential difference across each is the same.
  - the power dissipated in each is the same.
12. You have a  $5\ \Omega$  light bulb and a  $10\ \Omega$  light bulb. You make a circuit that places them in series across a battery. Which light bulb is brighter?
- The  $5\ \Omega$  bulb is brighter.
  - The  $10\ \Omega$  bulb is brighter.
  - Both bulbs glow at the same brightness.
  - It depends on the voltage.
13. A total of 713 resistors, all with resistance  $277\ \Omega$ , are connected in **parallel**. What is the equivalent resistance of the resistors?
- $0.3\ \Omega$
  - $0.24\ \Omega$
  - $0.39\ \Omega$
  - $0.49\ \Omega$
14. A total of 654 Christmas light bulbs, all with resistance  $350\ \Omega$ , are connected in **series**. What is the equivalent resistance of the lights?
- $190\text{ k}\Omega$
  - $160\text{ k}\Omega$
  - $130\text{ k}\Omega$
  - $230\text{ k}\Omega$

15. Two resistors are connected in **parallel**. Their resistances are  $441\ \Omega$  and  $335\ \Omega$ . A battery applies  $6.6\text{ V}$  to the combination. What is the current through the  $441\ \Omega$  resistor?
- $13\text{ mA}$
  - $15\text{ mA}$
  - $22\text{ mA}$
  - $26\text{ mA}$
16. Two resistors are connected in **series**. Their resistances are  $6\ \Omega$  and  $8\ \Omega$ . A difference in potential of  $73\text{ V}$  is applied to the combination. What is the current through the  $8\ \Omega$  resistor?
- $6.3\text{ A}$
  - $5.8\text{ A}$
  - $5.2\text{ A}$
  - $7.9\text{ A}$
17. Two resistors are connected in **parallel**. Their resistances are  $18\ \Omega$  and  $39\ \Omega$ . A battery applies  $39\text{ V}$  to the combination. What is the current drawn from the battery?
- $5.6\text{ A}$
  - $2.1\text{ A}$
  - $4.7\text{ A}$
  - $3.2\text{ A}$
18. Three resistors are connected in **parallel**. Their resistances are  $39\ \Omega$ ,  $74\ \Omega$ , and  $64\ \Omega$ . What is the equivalent resistance of the resistors?
- $12\ \Omega$
  - $18\ \Omega$
  - $16\ \Omega$
  - $14\ \Omega$
19. A  $800\text{ mA}$  current flows into a parallel combination of a  $44\ \Omega$  and a  $50\ \Omega$  resistor. What current flows through the  $44\ \Omega$  resistor?
- $850\text{ mA}$
  - $680\text{ mA}$
  - $580\text{ mA}$
  - $430\text{ mA}$
20. When a battery with an emf of  $5\text{ V}$  supplies a  $9.8\text{ A}$  current, its terminal voltage is  $4.4\text{ V}$ . What is the internal resistance of the battery?
- $0.047\ \Omega$
  - $0.033\ \Omega$
  - $0.055\ \Omega$
  - $0.061\ \Omega$